

CS 61C:
Great Ideas in Computer Architecture
Single-Cycle CPU
Datapath & Control


Instructors:

John Wawrzynek & Vladimir Stojanovic


<http://inst.eecs.Berkeley.edu/~cs61c/fa15>

Step 3b: Add & Subtract

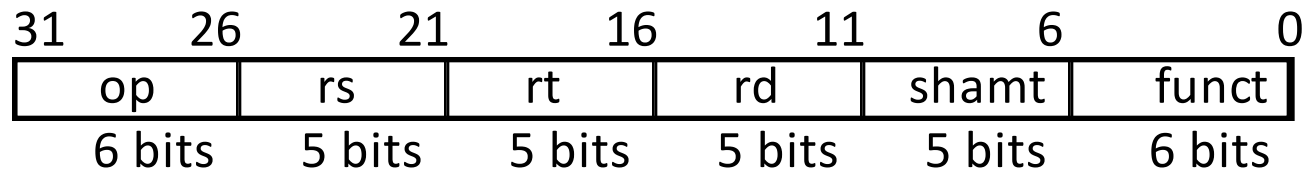- $R[rd] = R[rs] \text{ op } R[rt]$ (`addu rd,rs,rt`)
 - Ra, Rb, and Rw come from instruction's Rs, Rt, and Rd fields




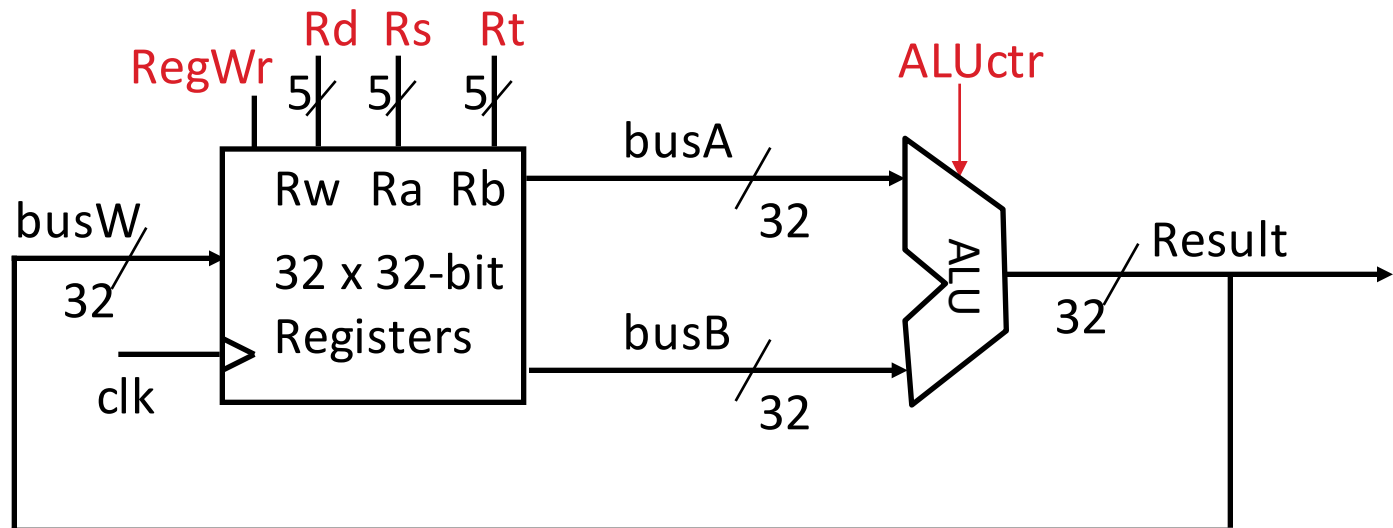- **ALUctr** and **RegWr**: control logic after decoding the instruction





- ... Already defined the register file & ALU

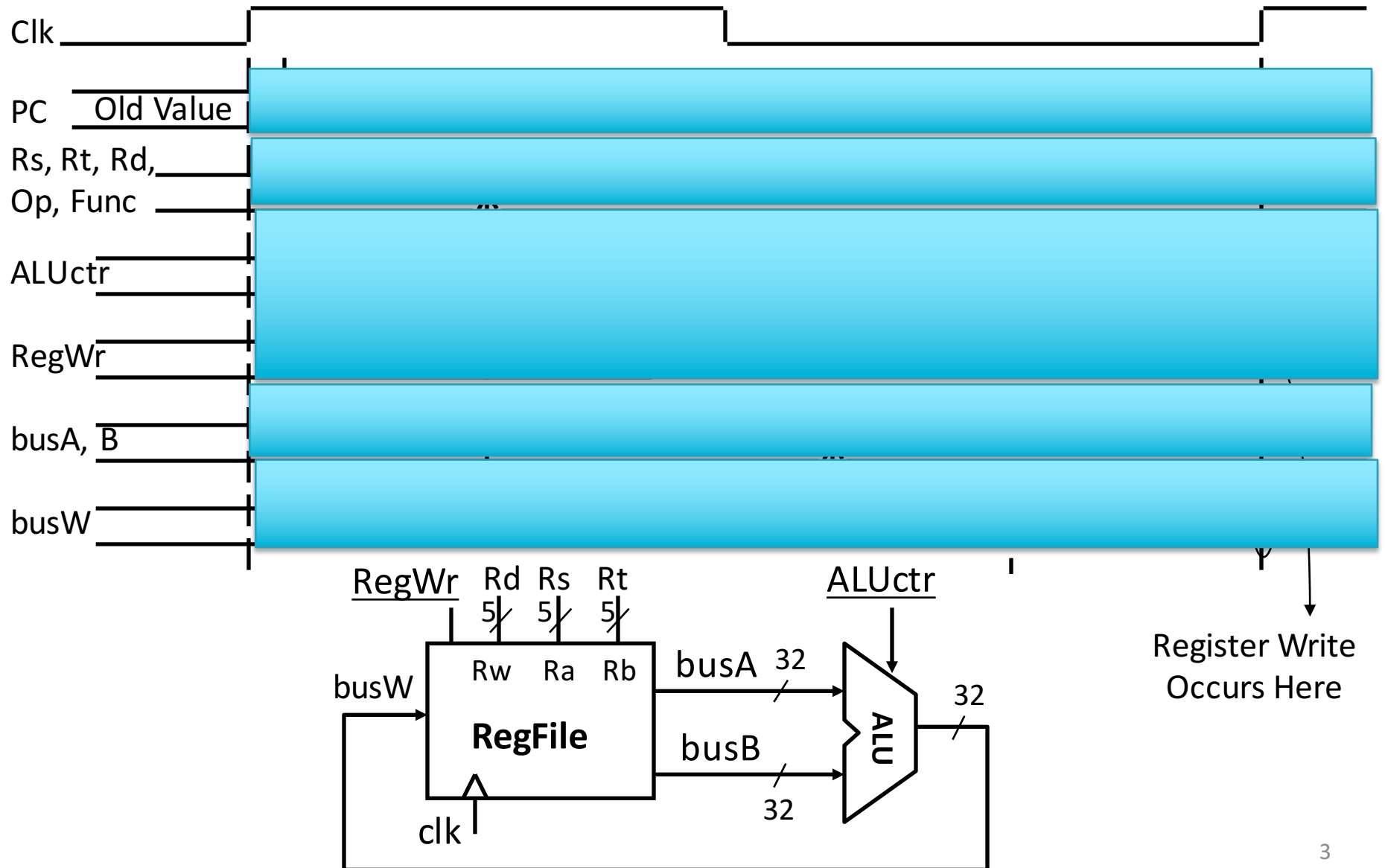Register-Register Timing: One Complete Cycle (Add/Sub)



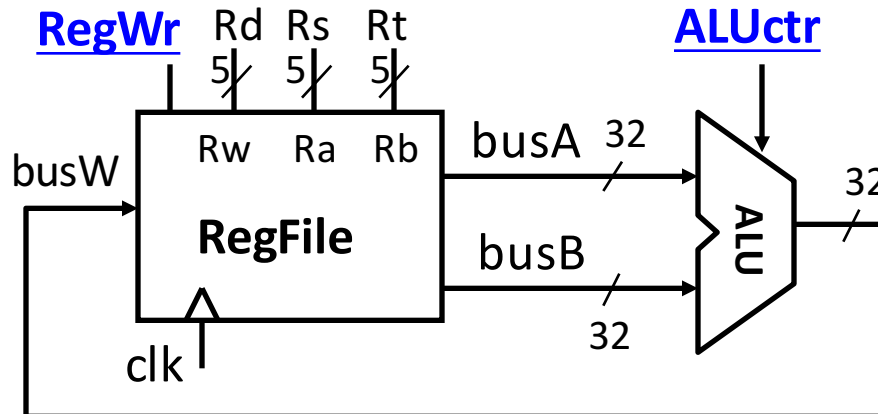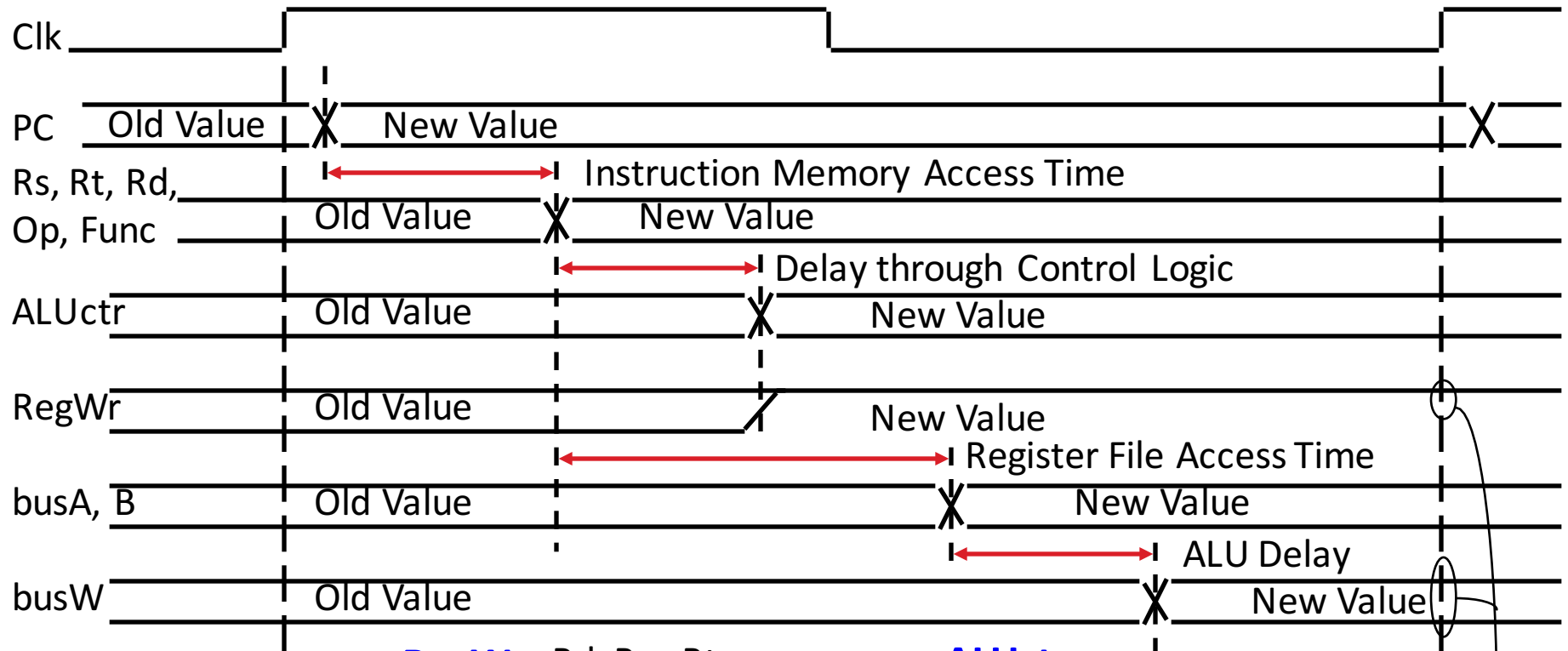
Register-Register Timing: One Complete Cycle



Register Write
Occurs Here

3c: Logical Op (or) with Immediate

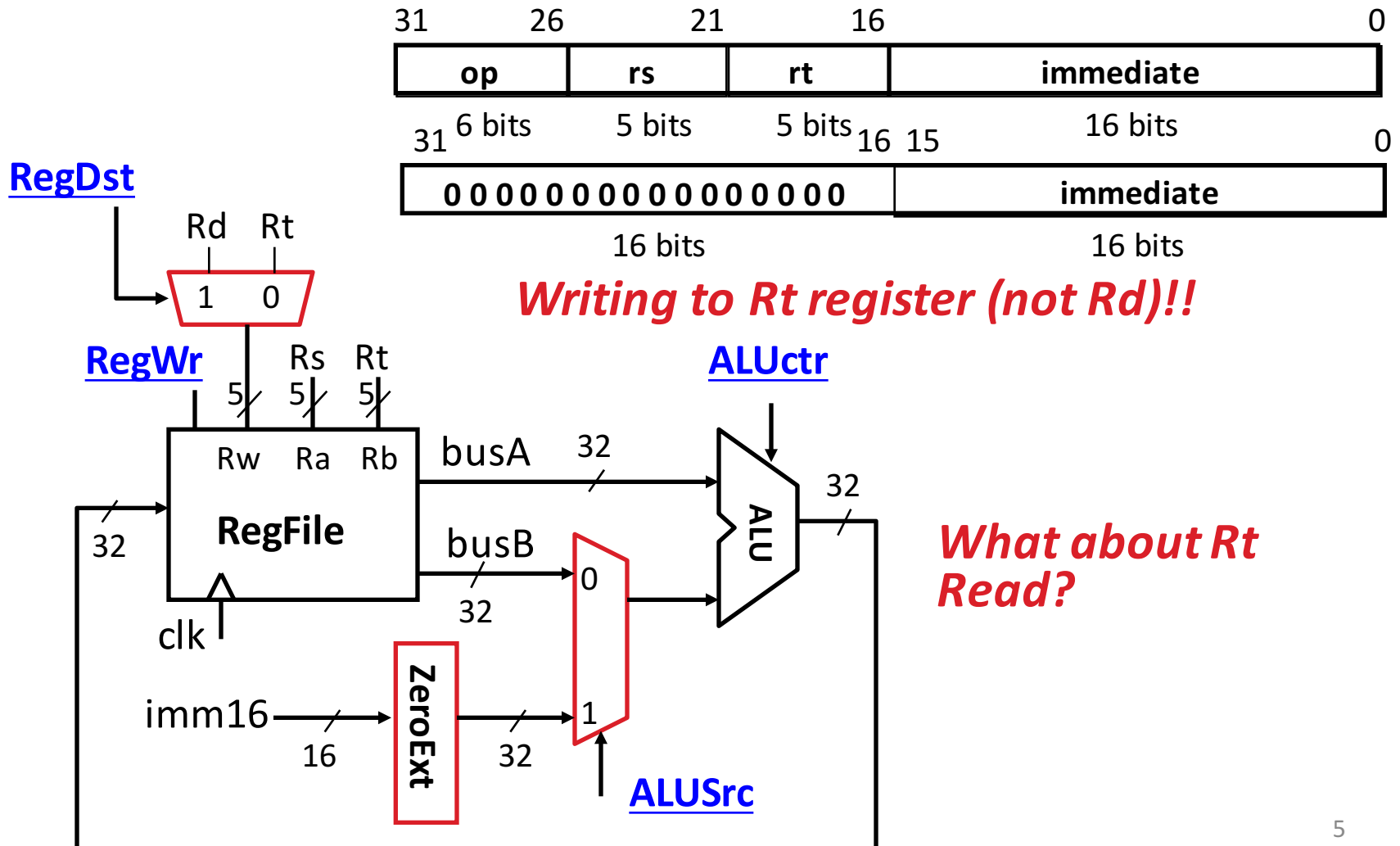
- $R[\text{rt}] = R[\text{rs}] \text{ op ZeroExt}[\text{imm16}]$



3d: Load Operations

- $R[\text{rt}] = \text{Mem}[R[\text{rs}] + \text{SignExt}[\text{imm16}]]$



Example: `lw rt, rs, imm16`

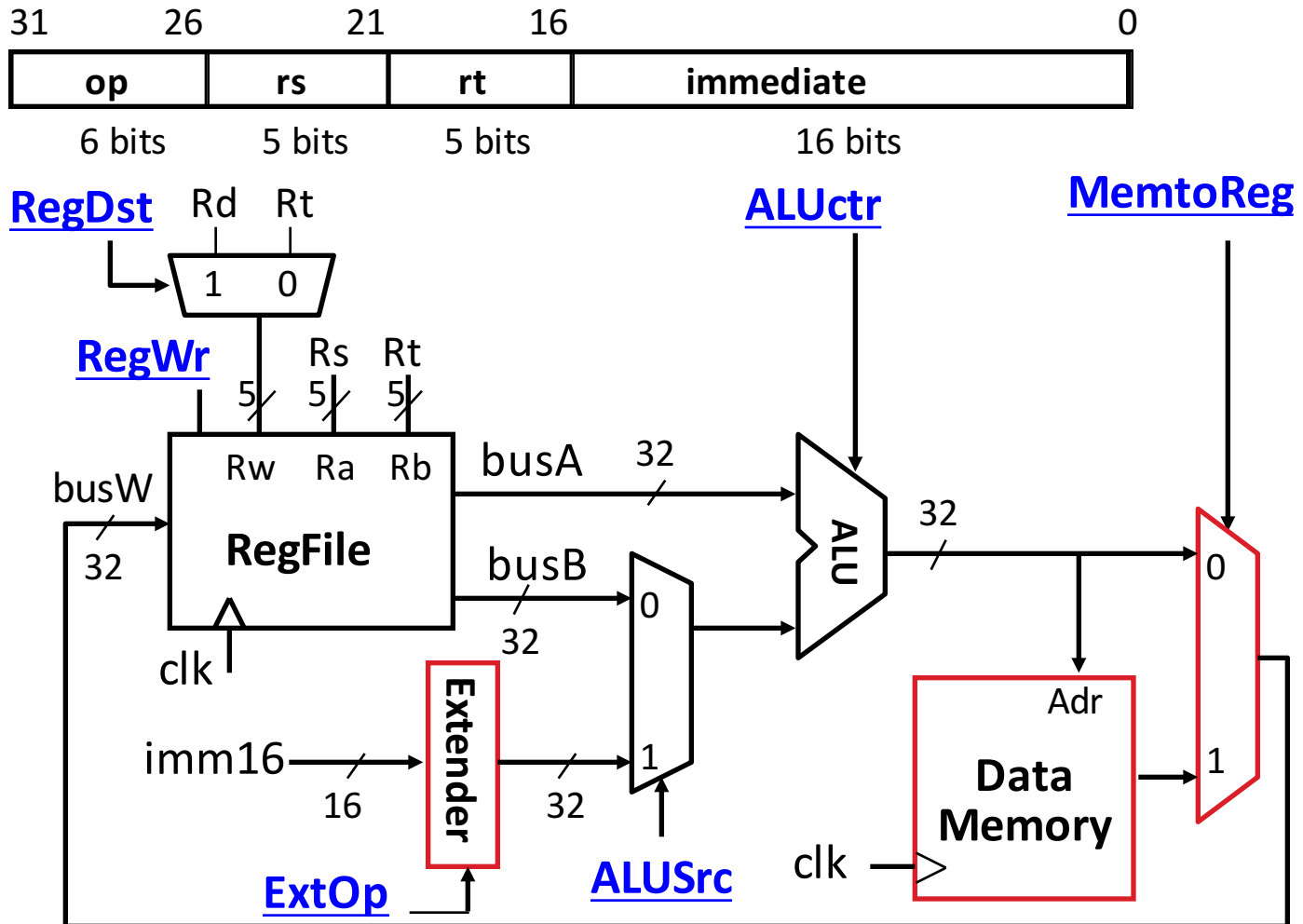

3e: Store Operations

- Mem[R[rs] + SignExt[imm16]] = R[rt]



Ex.: sw rt, rs, imm16

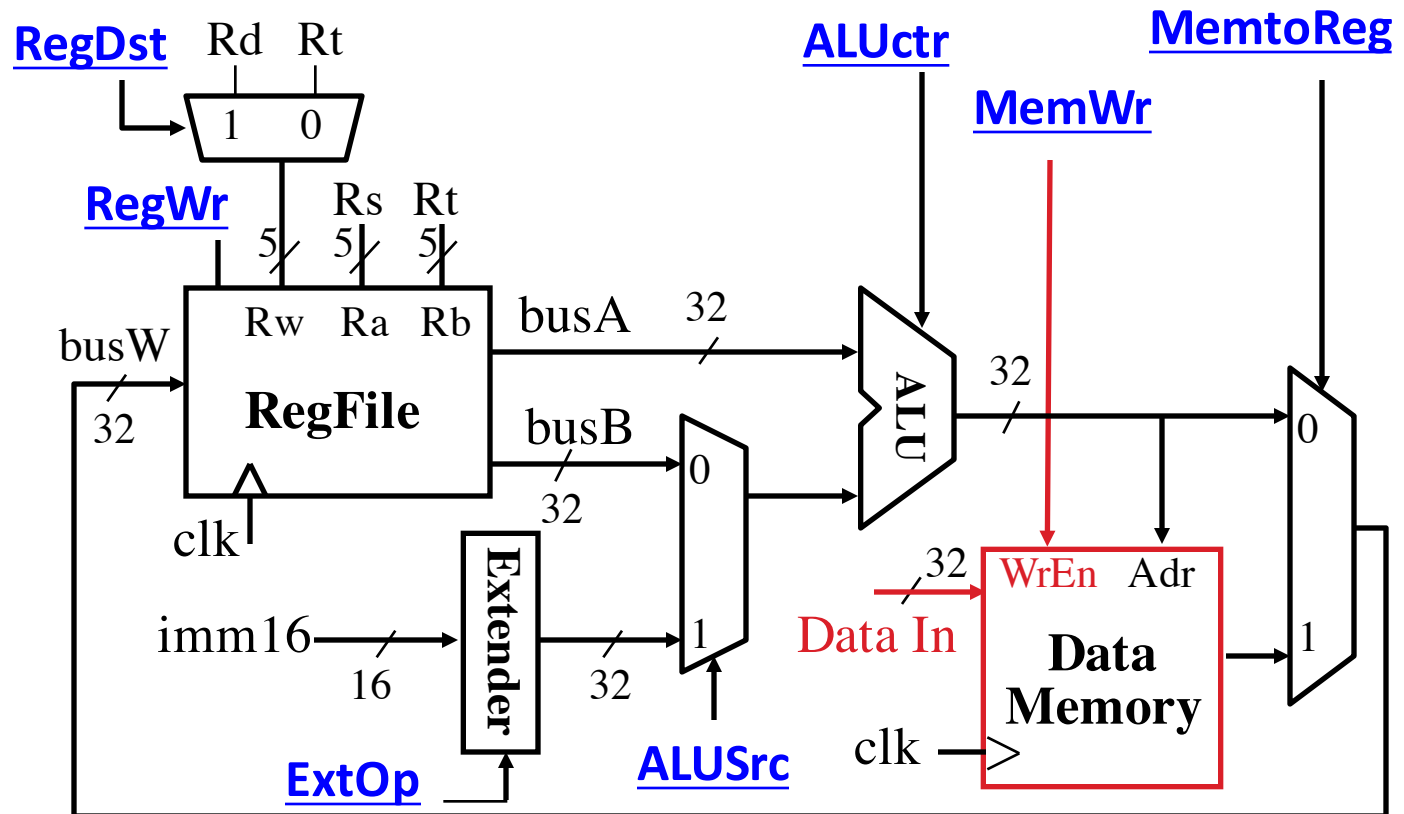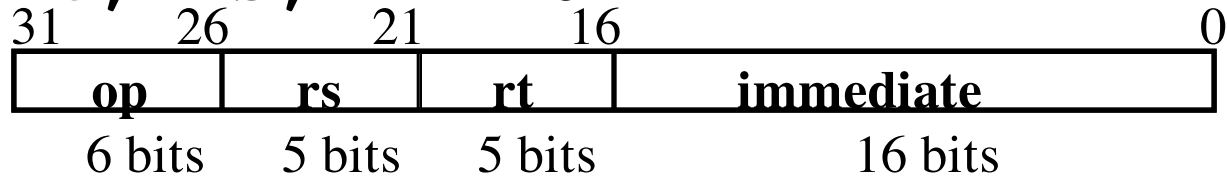


3e: Store Operations

- Mem[R[rs] + SignExt[imm16]] = R[rt]

Ex.: sw rt, rs, imm16

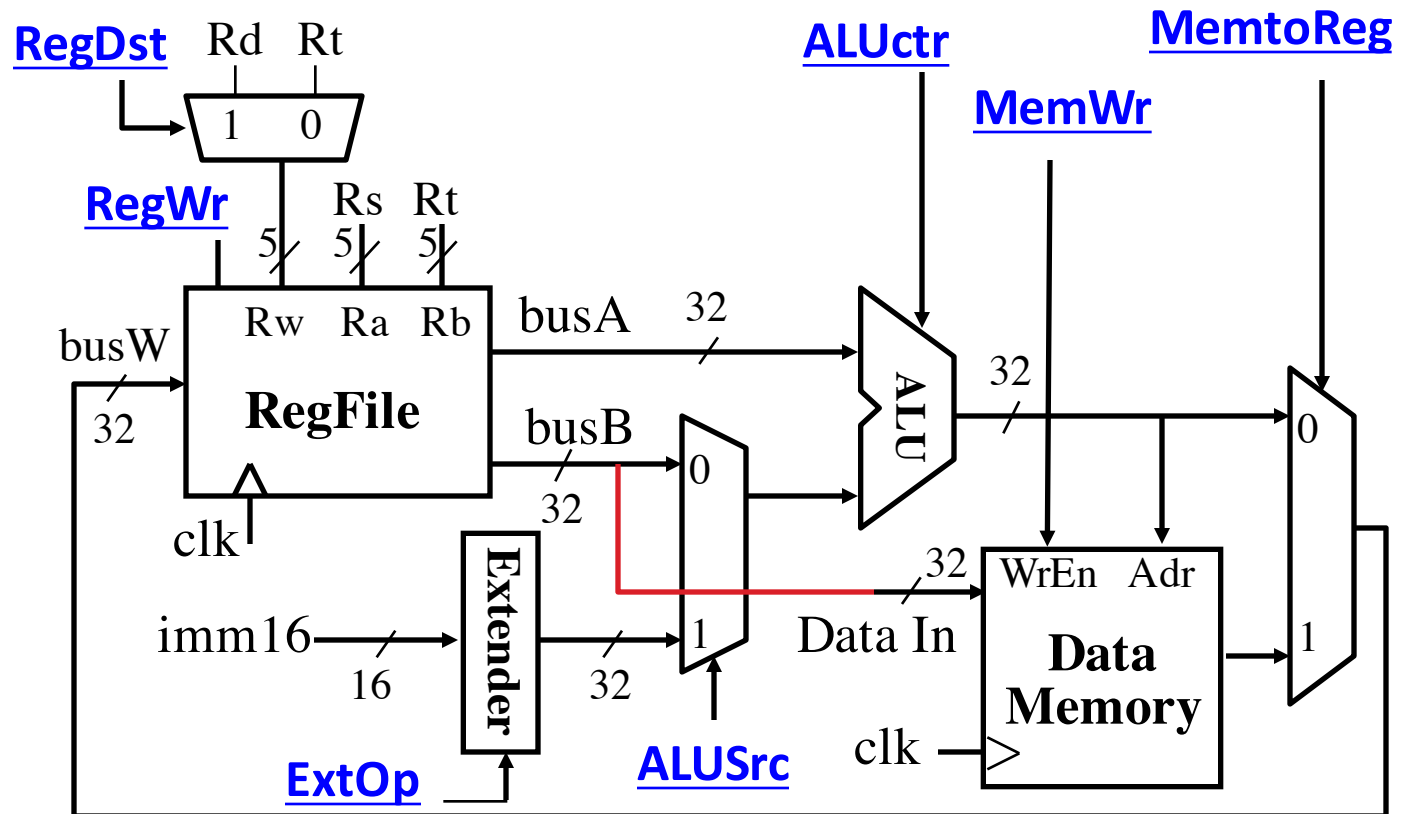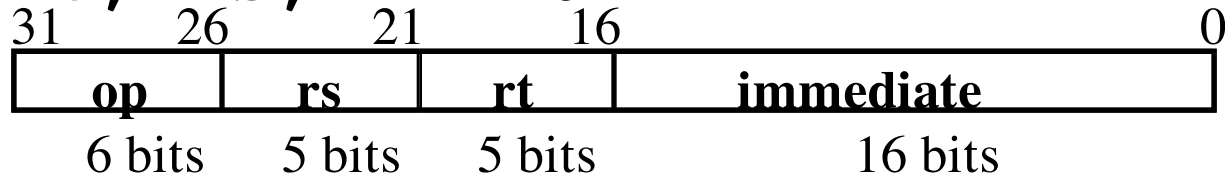

3f: The Branch Instruction

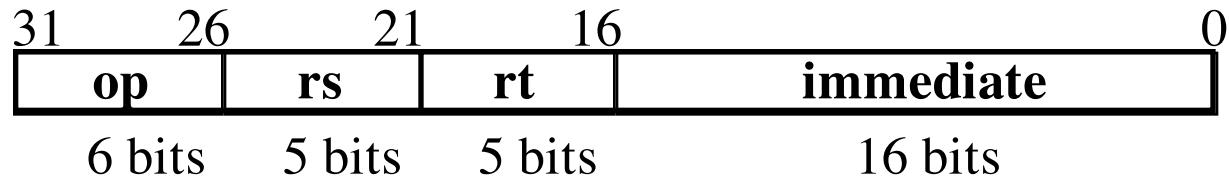

`beq rs, rt, imm16`


- `mem[PC]` Fetch the instruction from memory
- `Equal = (R[rs] == R[rt])` Calculate branch condition
- if (`Equal`) Calculate the next instruction's address
 - $PC = PC + 4 + (\text{SignExt}(\text{imm16}) \times 4)$

else

- $PC = PC + 4$


Datapath for Branch Operations

beq rs, rt, imm16

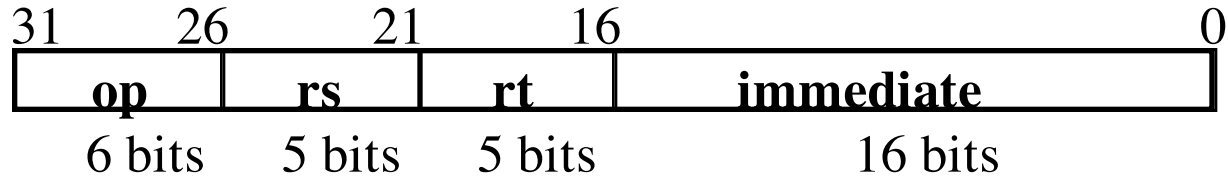


Datapath generates condition (Equal)

Inst Address

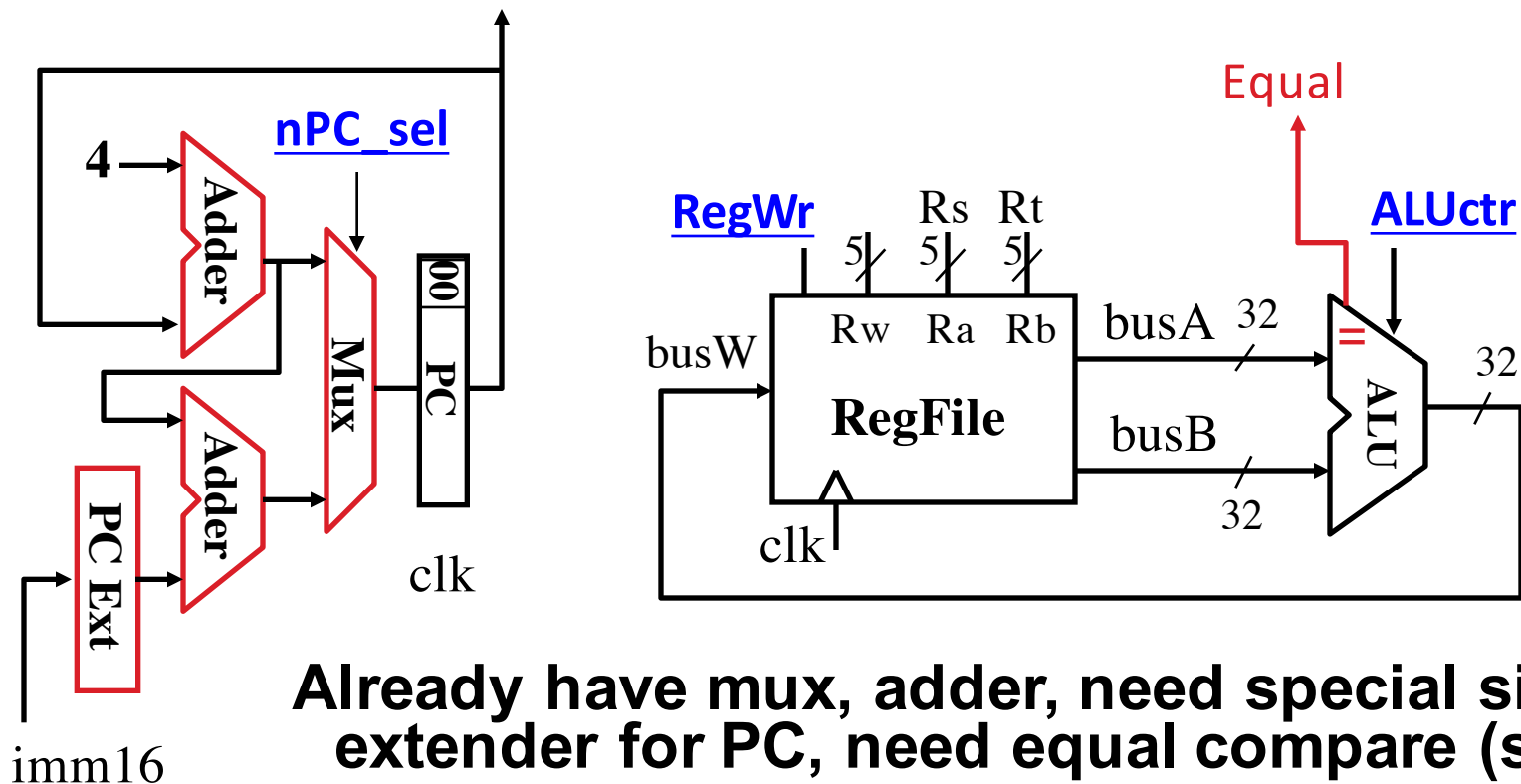


Already have mux, adder, need special sign extender for PC, need equal compare (sub?)

Instruction Fetch Unit including Branch

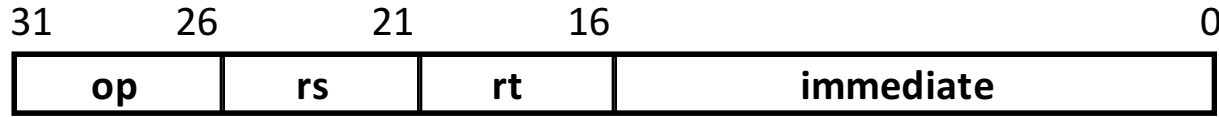

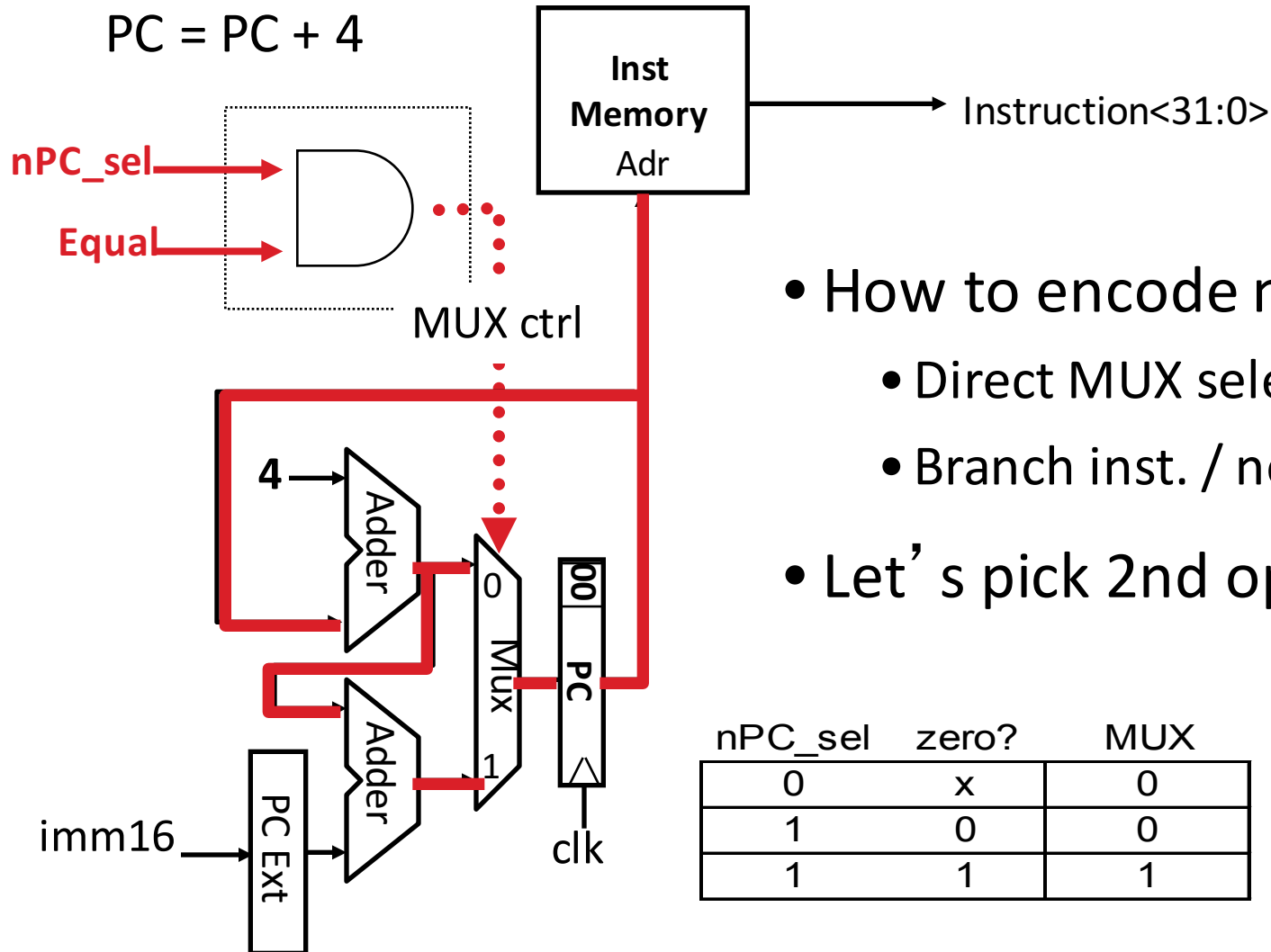- if (Zero == 1) then $PC = PC + 4 + \text{SignExt}[\text{imm16}] * 4$; else $PC = PC + 4$




- How to encode nPC_sel?
 - Direct MUX select?
 - Branch inst. / not branch inst.
- Let's pick 2nd option

nPC_sel	zero?	MUX
0	x	0
1	0	0
1	1	1

Q: What logic gate?



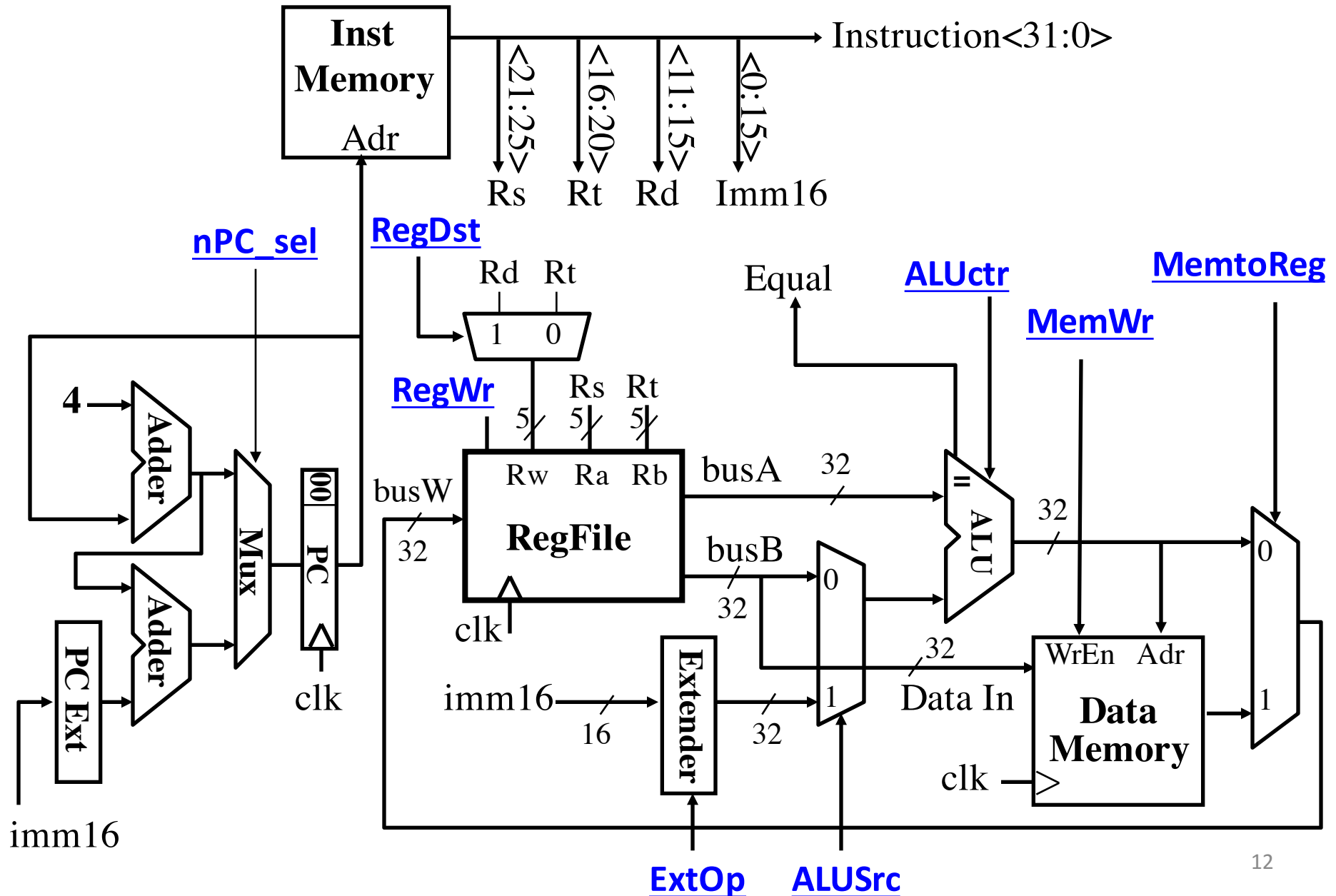
Putting it All Together: A Single Cycle Datapath



Clickers/Peer Instruction

What new instruction would need no new datapath hardware?

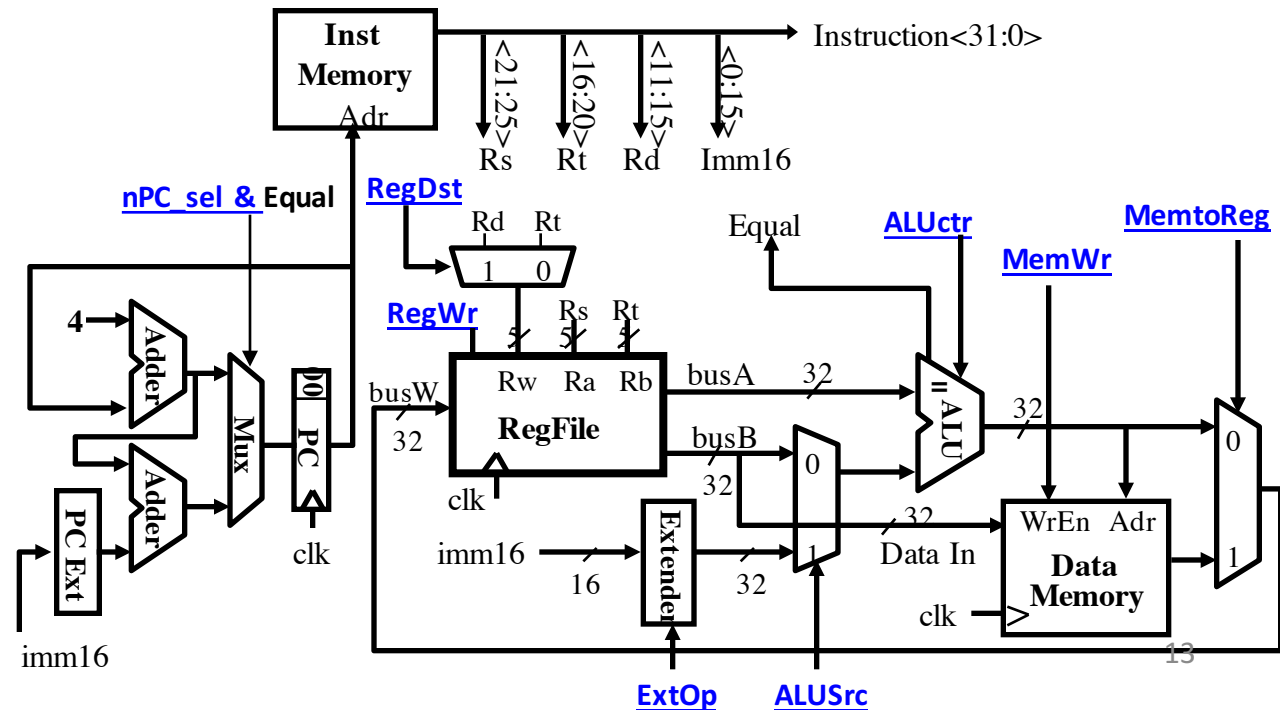- A: branch if reg==immediate
- B: add two registers and branch if result zero
- C: store with auto-increment of base address:
 - sw rt, rs, offset // rs incremented by offset after store
- D: shift left logical by one bit



Administrivia

- Midterm
 - A: Super Hard
 - ...
 - E: Too Easy
- Project 2-2 due 10/11
 - A: Haven't started
 - B: Done with Step 1
 - C: Done with Step 2
 - D: Done with Step 3
 - E: Finished

Processor Design: 5 steps

Step 1: Analyze instruction set to determine datapath requirements

- Meaning of each instruction is given by register transfers
- Datapath must include storage element for ISA registers
- Datapath must support each register transfer

Step 2: Select set of datapath components & establish clock methodology


Step 3: Assemble datapath components that meet the requirements

Step 4: Analyze implementation of each instruction to determine setting of control points that realizes the register transfer


Step 5: Assemble the control logic

Datapath Control Signals

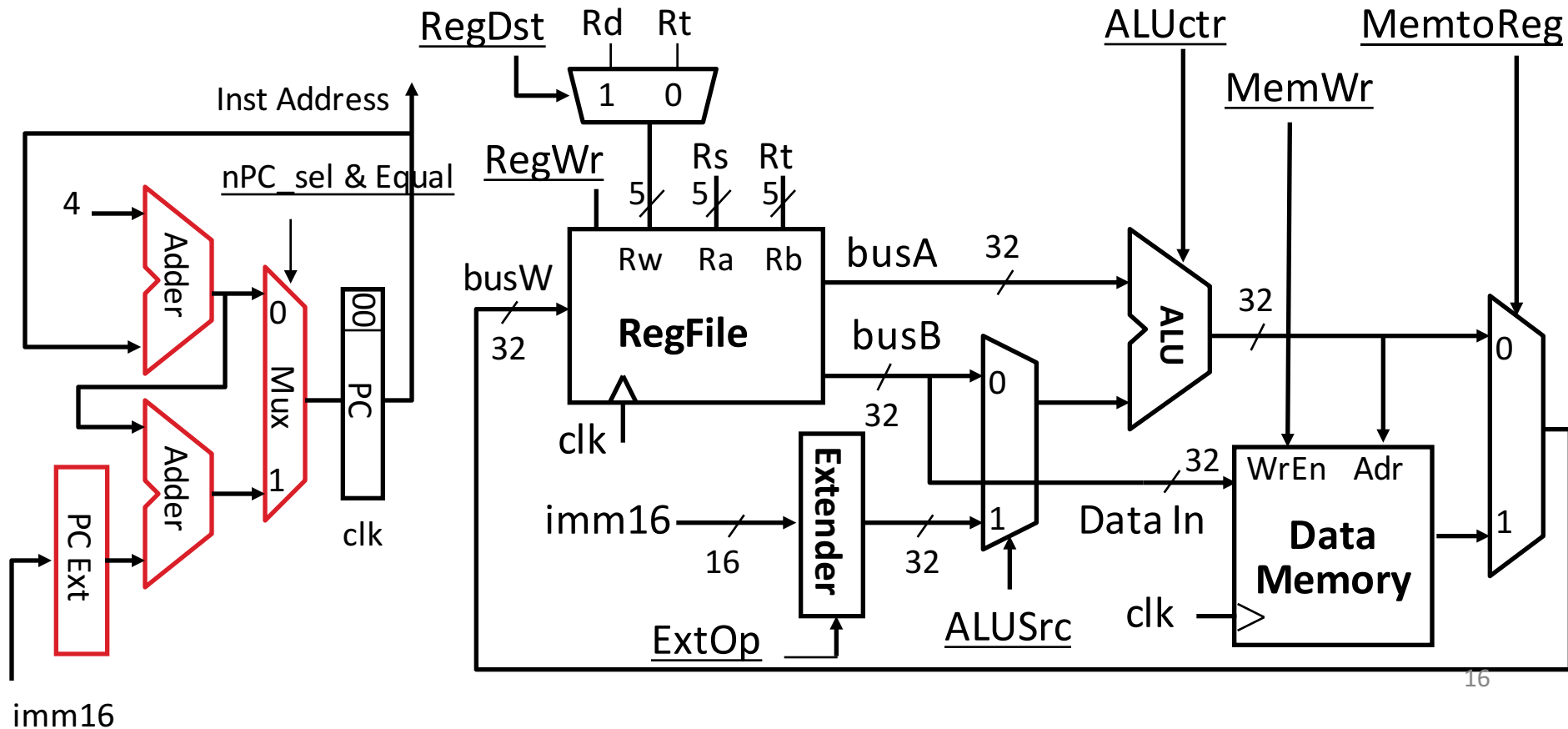
- ExtOp: “zero”, “sign”
- ALUsrc: 0 \Rightarrow regB;
1 \Rightarrow immedi
- ALUctr: “ADD”, “SUB”, “OR”
- MemWr: 1 \Rightarrow write memory
- MemtoReg: 0 \Rightarrow ALU; 1 \Rightarrow Mem
- RegDst: 0 \Rightarrow “rt”; 1 \Rightarrow “rd”
- RegWr: 1 \Rightarrow write register



Given Datapath: RTL \rightarrow Control

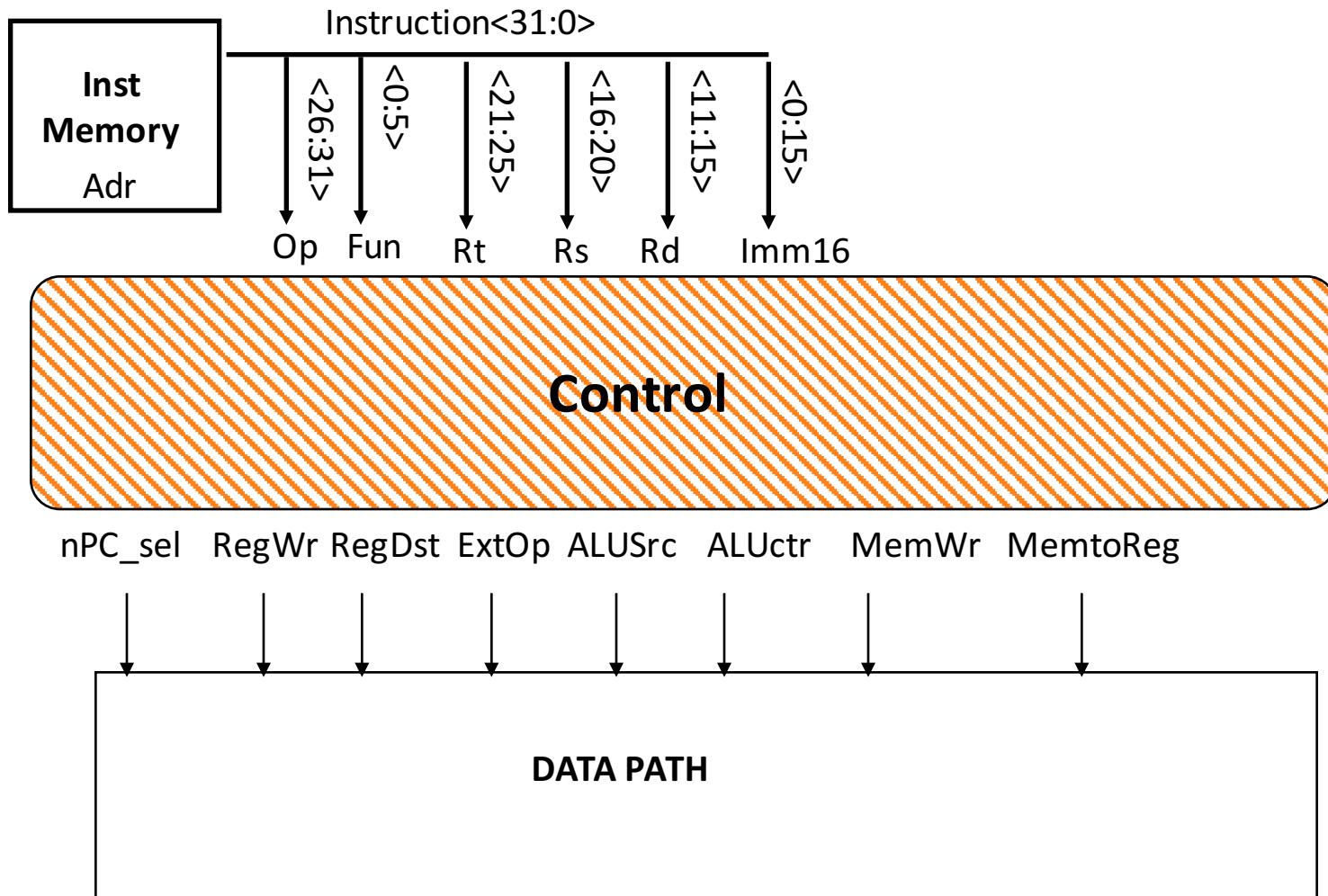

RTL: The Add Instruction

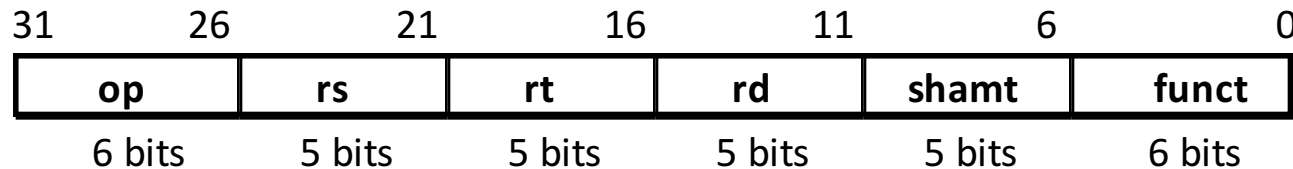


add rd, rs, rt

- MEM[PC] Fetch the instruction from memory
- $R[rd] = R[rs] + R[rt]$ The actual operation
- $PC = PC + 4$ Calculate the next instruction's address


Instruction Fetch Unit at the Beginning of Add

- Fetch the instruction from Instruction memory: $\text{Instruction} = \text{MEM}[\text{PC}]$


– same for all instructions

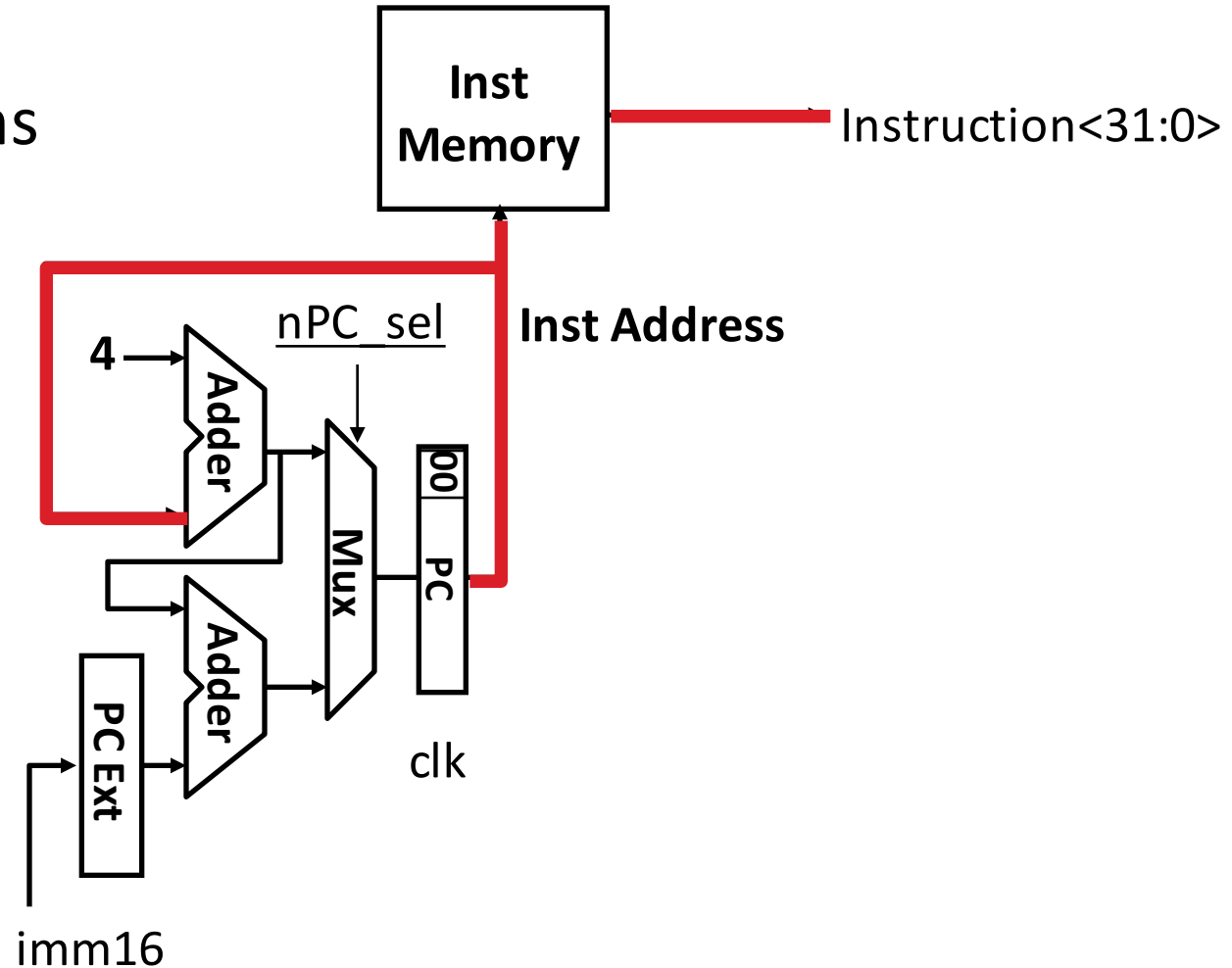

Single Cycle Datapath during Add

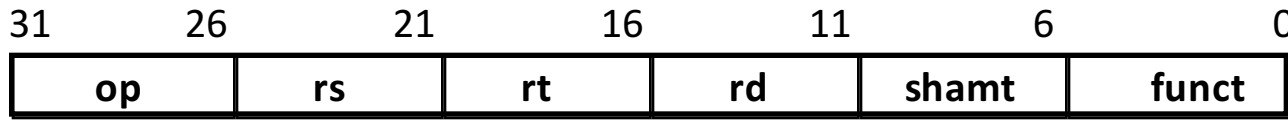


$$R[rd] = R[rs] + R[rt]$$

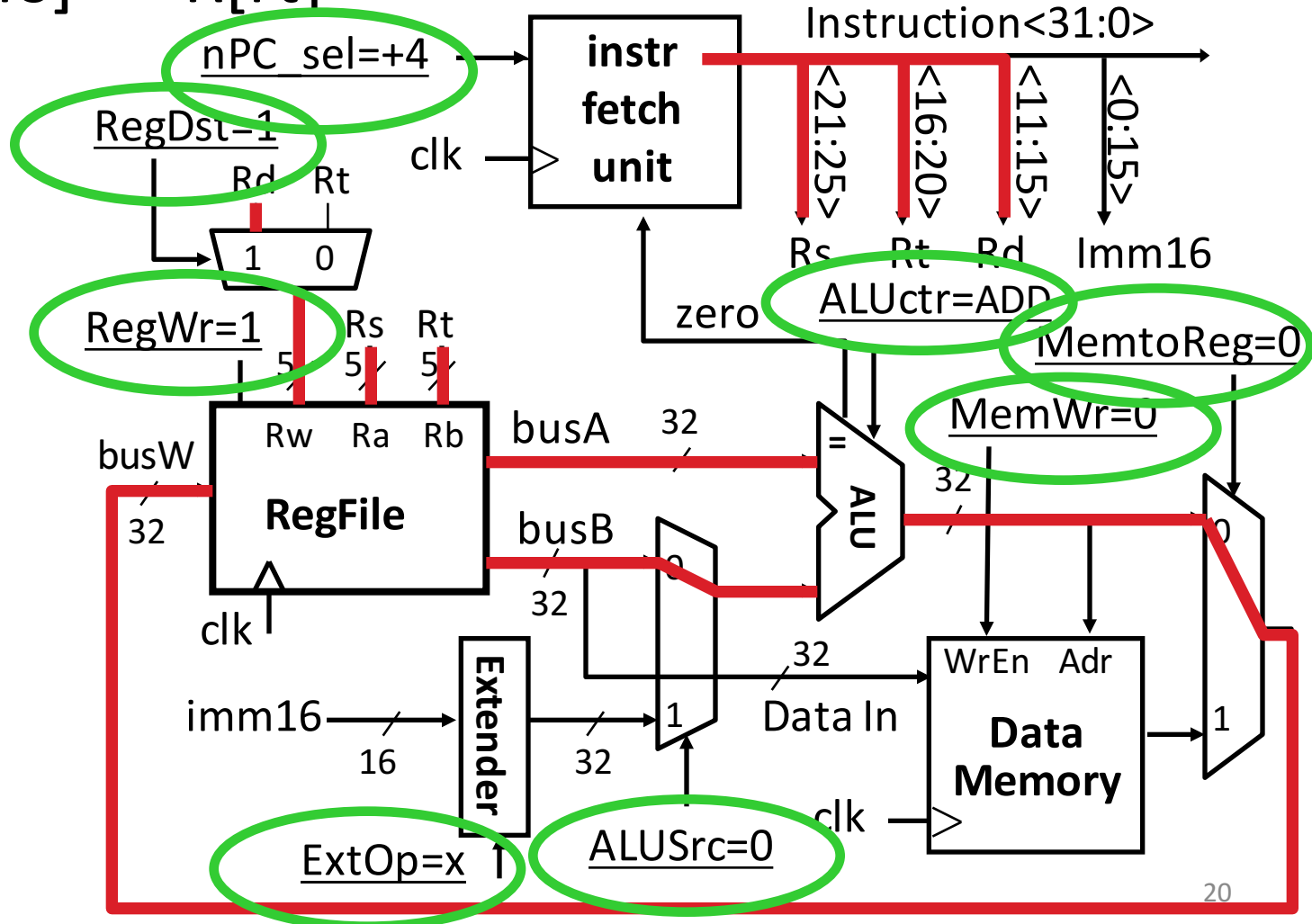

Instruction Fetch Unit at End of Add

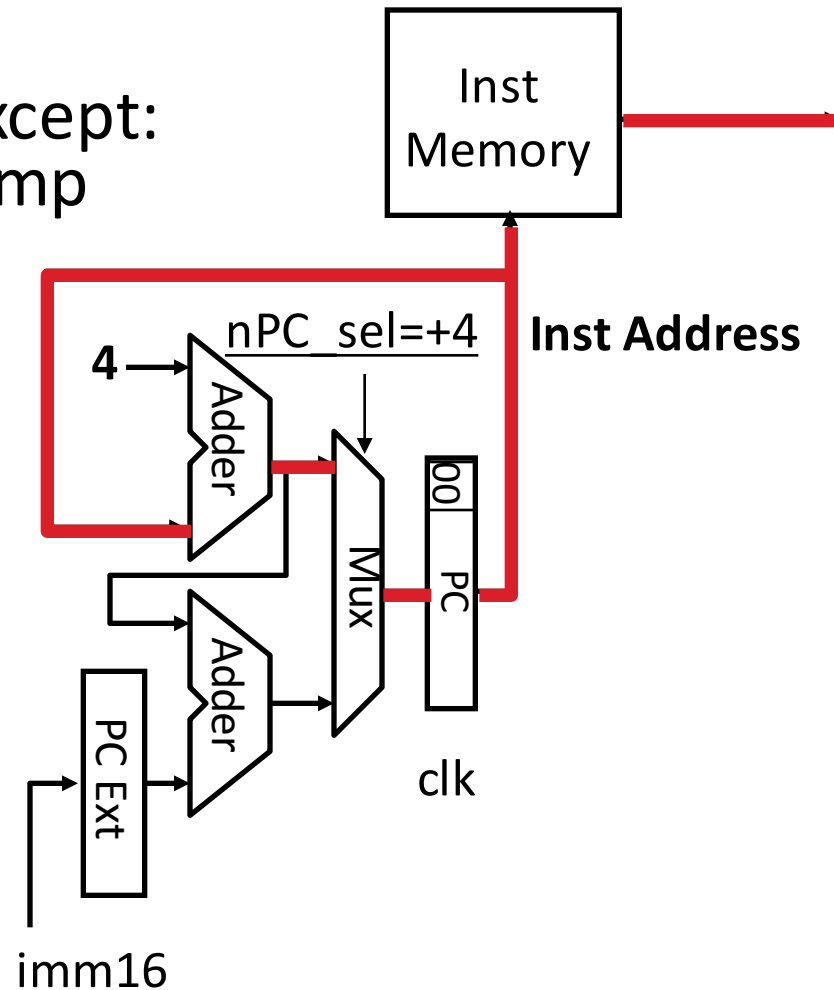
- $PC = PC + 4$
 - Same for all instructions except:
Branch and Jump



Single Cycle Datapath during Jump



 
- New PC = { PC[31..28], target address, 00 }



Single Cycle Datapath during Jump



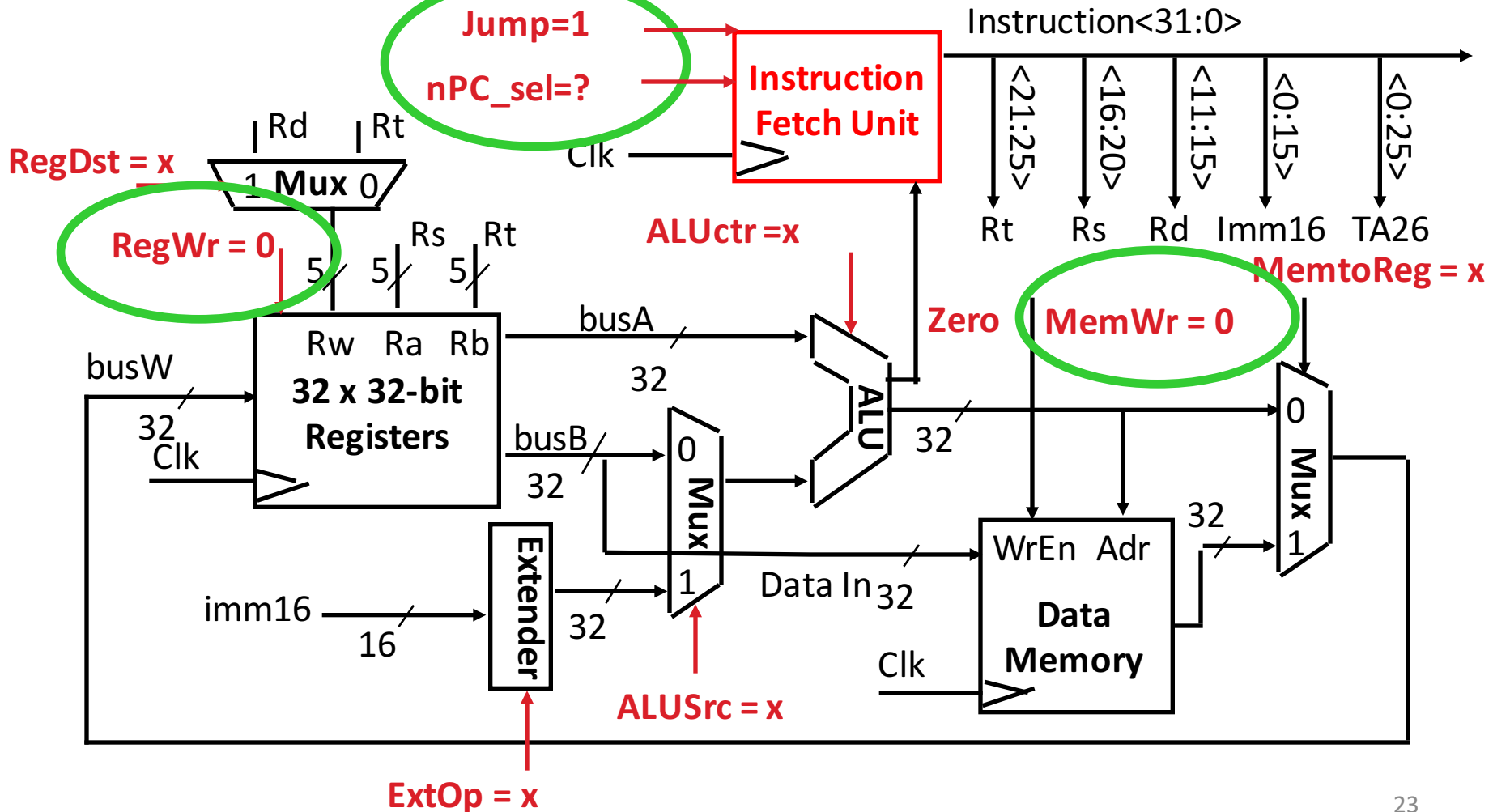
- New PC = { PC[31..28], target address, 00 }



Instruction Fetch Unit at the End of Jump




 - New PC = { PC[31..28], target address, 00 }



How do we modify this to account for jumps?

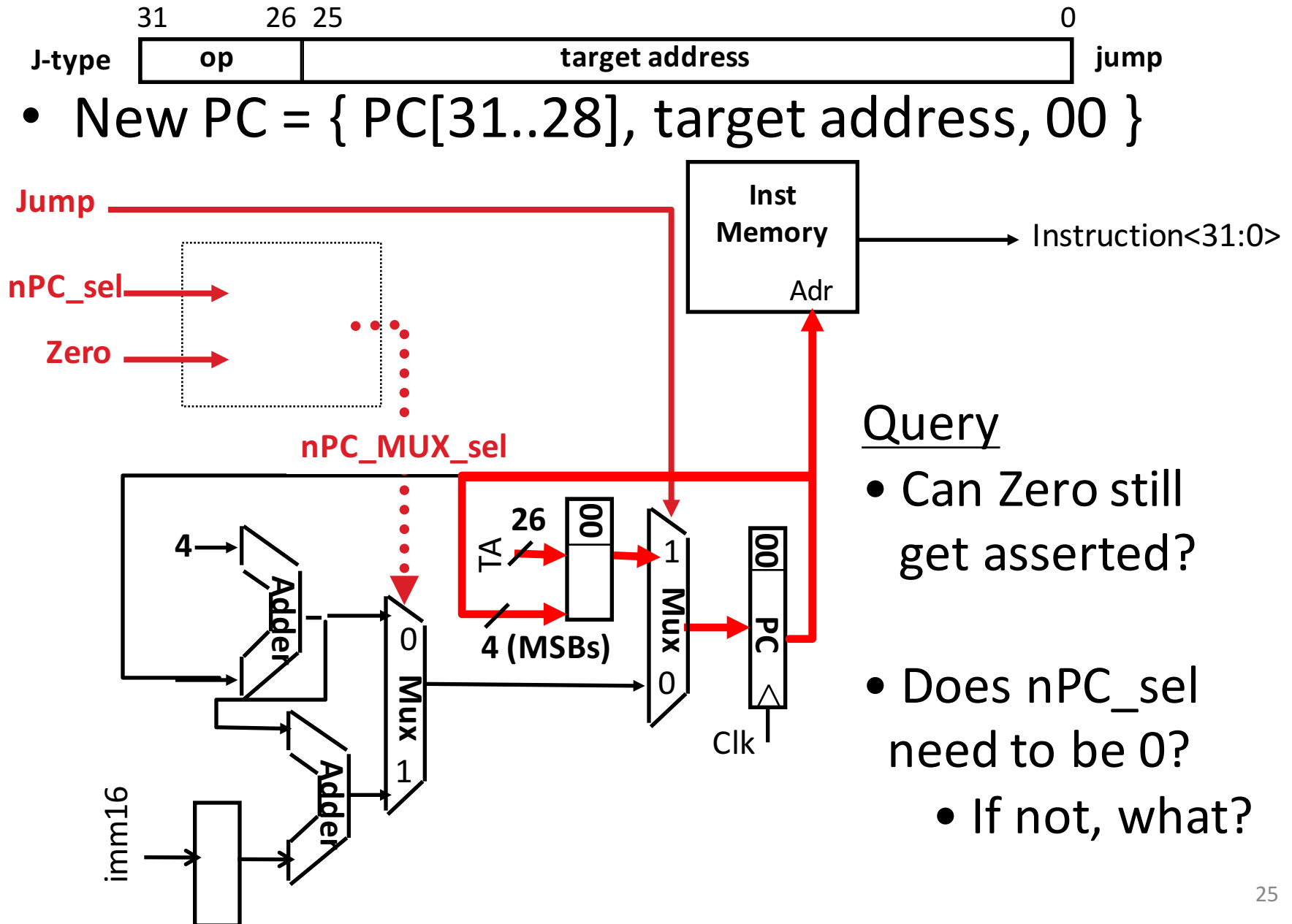Instruction Fetch Unit at the End of Jump




Clicker Question

Which of the following is TRUE?

- A. The clock can have a shorter period for instructions that don't use memory
- B. The ALU is used to set PC to PC+4 when necessary
- C. Worst-delay path in Instruction Fetch unit is Add+mux delay
- D. The CPU's control needs only *opcode* to determine the next PC value to select
- E. `npc_sel` affects the next PC address on a *jump*

In The News: Tile-Mx100

100 64-bit ARM cores on one chip

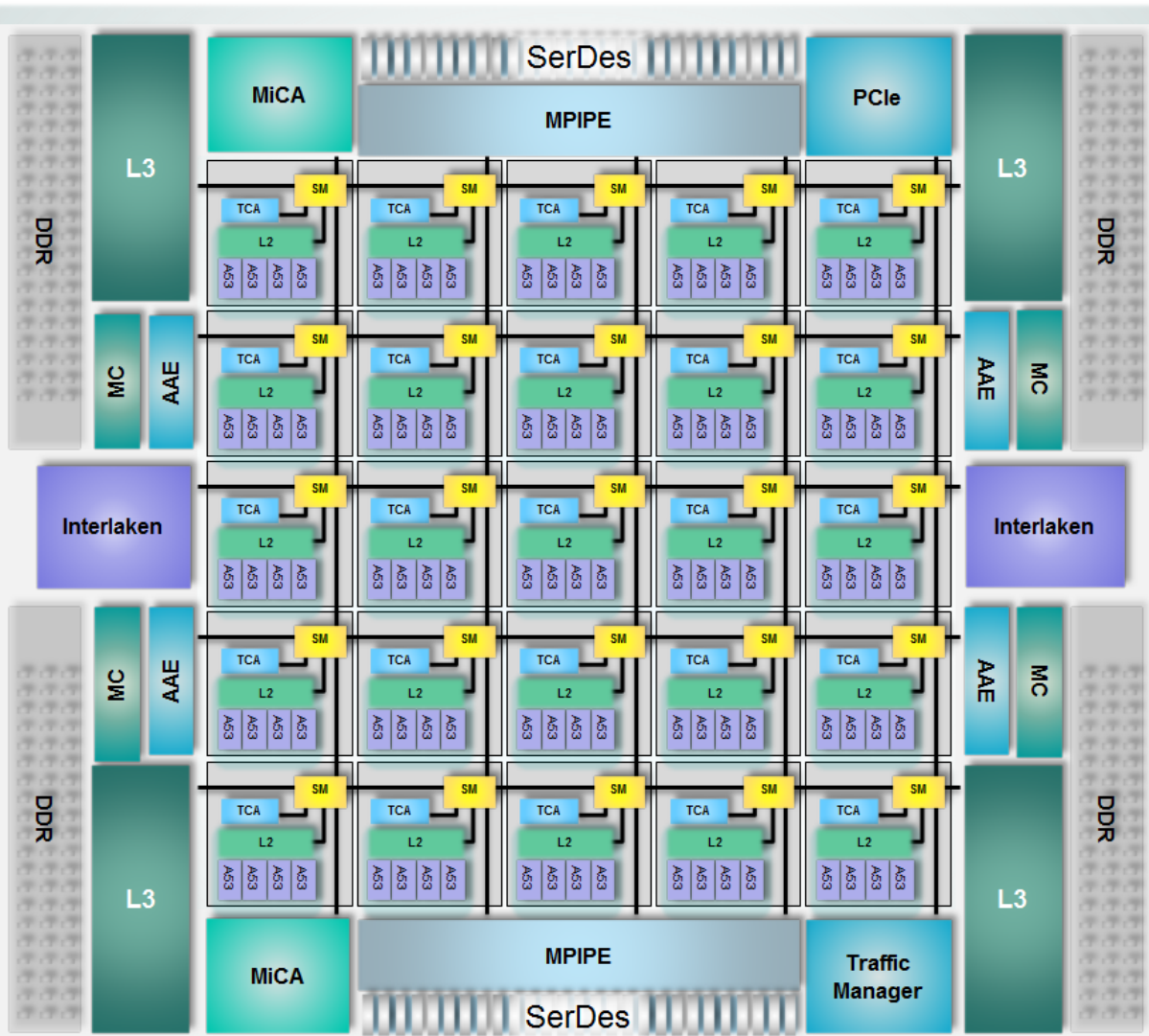

EZChip (bought Tiler)

100 64-bit ARM Cortex A53

- Dual-issue, in-order

Summary of the Control Signals (1/2)

<u>inst</u>	<u>Register Transfer</u>
add	$R[rd] \leftarrow R[rs] + R[rt]; PC \leftarrow PC + 4$ $ALUsrc=RegB, ALUctr="ADD", RegDst=rd, RegWr, nPC_sel="+4"$
sub	$R[rd] \leftarrow R[rs] - R[rt]; PC \leftarrow PC + 4$ $ALUsrc=RegB, ALUctr="SUB", RegDst=rd, RegWr, nPC_sel="+4"$
ori	$R[rt] \leftarrow R[rs] + zero_ext(Imm16); PC \leftarrow PC + 4$ $ALUsrc=Im, Extop="Z", ALUctr="OR", RegDst=rt, RegWr, nPC_sel="+4"$
lw	$R[rt] \leftarrow MEM[R[rs] + sign_ext(Imm16)]; PC \leftarrow PC + 4$ $ALUsrc=Im, Extop="sn", ALUctr="ADD", MemtoReg, RegDst=rt, RegWr, nPC_sel = "+4"$
sw	$MEM[R[rs] + sign_ext(Imm16)] \leftarrow R[rs]; PC \leftarrow PC + 4$ $ALUsrc=Im, Extop="sn", ALUctr = "ADD", MemWr, nPC_sel = "+4"$
beq	$if (R[rs] == R[rt]) then PC \leftarrow PC + sign_ext(Imm16) 00$ $else PC \leftarrow PC + 4$ $nPC_sel = "br", ALUctr = "SUB"$

Summary of the Control Signals (2/2)

See Appendix A

func

op

	10 0000	10 0010	We Don't Care :-)				
	00 0000	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	add	sub	ori	lw	sw	beq	jump
RegDst	1	1	0	0	x	x	x
ALUSrc	0	0	1	1	1	0	x
MemtoReg	0	0	0	1	x	x	x
RegWrite	1	1	1	1	0	0	0
MemWrite	0	0	0	0	1	0	0
nPCsel	0	0	0	0	0	1	?
Jump	0	0	0	0	0	0	1
ExtOp	x	x	0	1	1	x	x
ALUctr<2:0>	Add	Subtract	Or	Add	Add	Subtract	x

	31	26	21	16	11	6	0						
R-type	op		rs		rt		rd		shamt		funct		add, sub
I-type	op		rs		rt		immediate						ori, lw, sw, beq
J-type	op		target address										jump

Boolean Expressions for Controller

```
RegDst      = add + sub
ALUSrc      = ori + lw + sw
MemtoReg    = lw
RegWrite    = add + sub + ori + lw
MemWrite    = sw
nPCsel      = beq
Jump        = jump
ExtOp       = lw + sw
ALUctr[0]   = sub + beq    (assume ALUctr is 00 ADD, 01 SUB, 10 OR)
ALUctr[1]   = or
```


Where:

```
rtype = ~op5 • ~op4 • ~op3 • ~op2 • ~op1 • ~op0,
ori    = ~op5 • ~op4 • op3 • op2 • ~op1 • op0
lw     = op5 • ~op4 • ~op3 • ~op2 • op1 • op0
sw     = op5 • ~op4 • op3 • ~op2 • op1 • op0
beq    = ~op5 • ~op4 • ~op3 • op2 • ~op1 • ~op0
jump   = ~op5 • ~op4 • ~op3 • ~op2 • op1 • ~op0
```


```
add = rtype • func5 • ~func4 • ~func3 • ~func2 • ~func1 • ~func0
sub = rtype • func5 • ~func4 • ~func3 • ~func2 • func1 • ~func0
```

How do we
implement this in
gates?

Controller Implementation

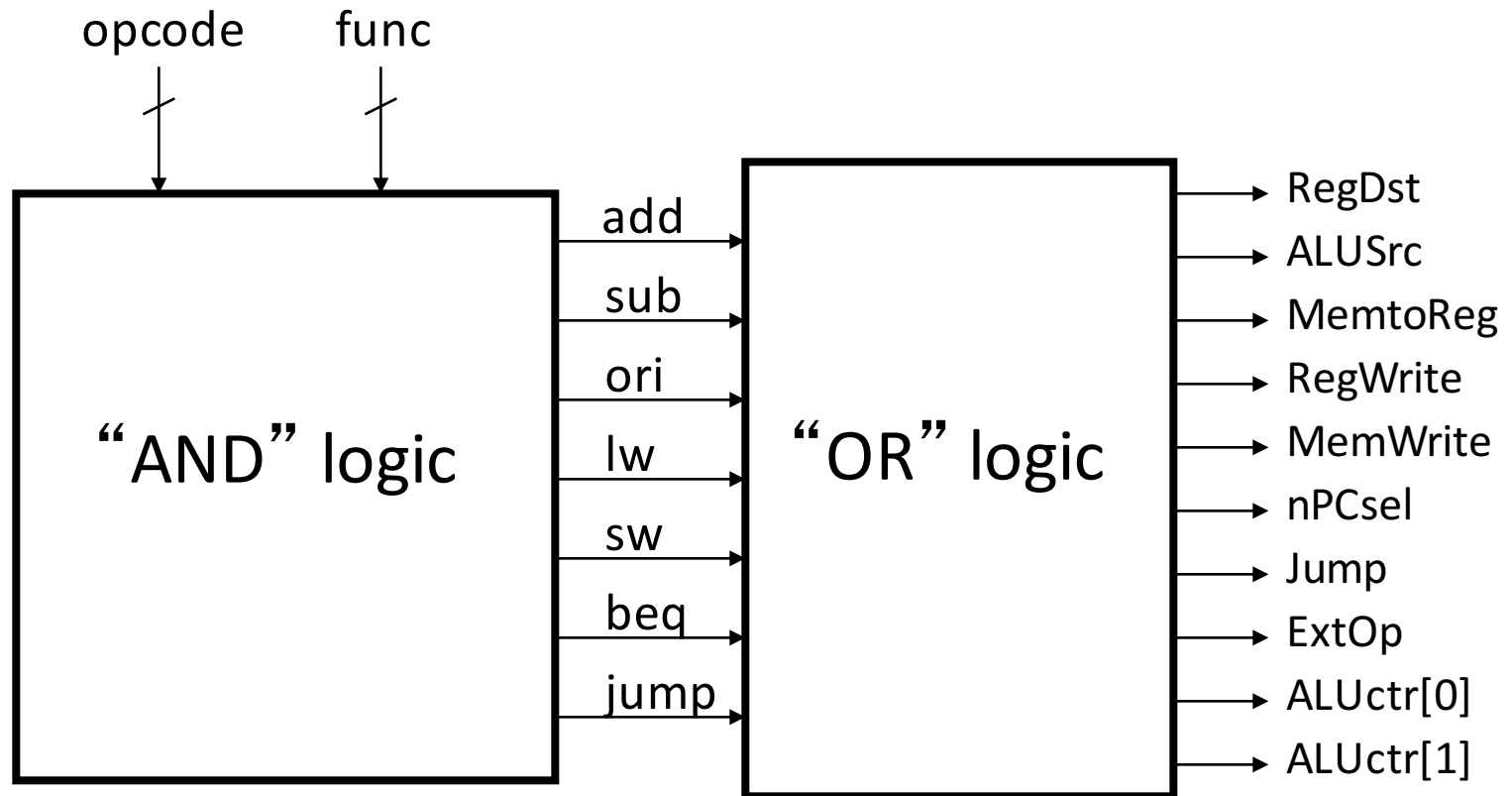


P&H Figure 4.17

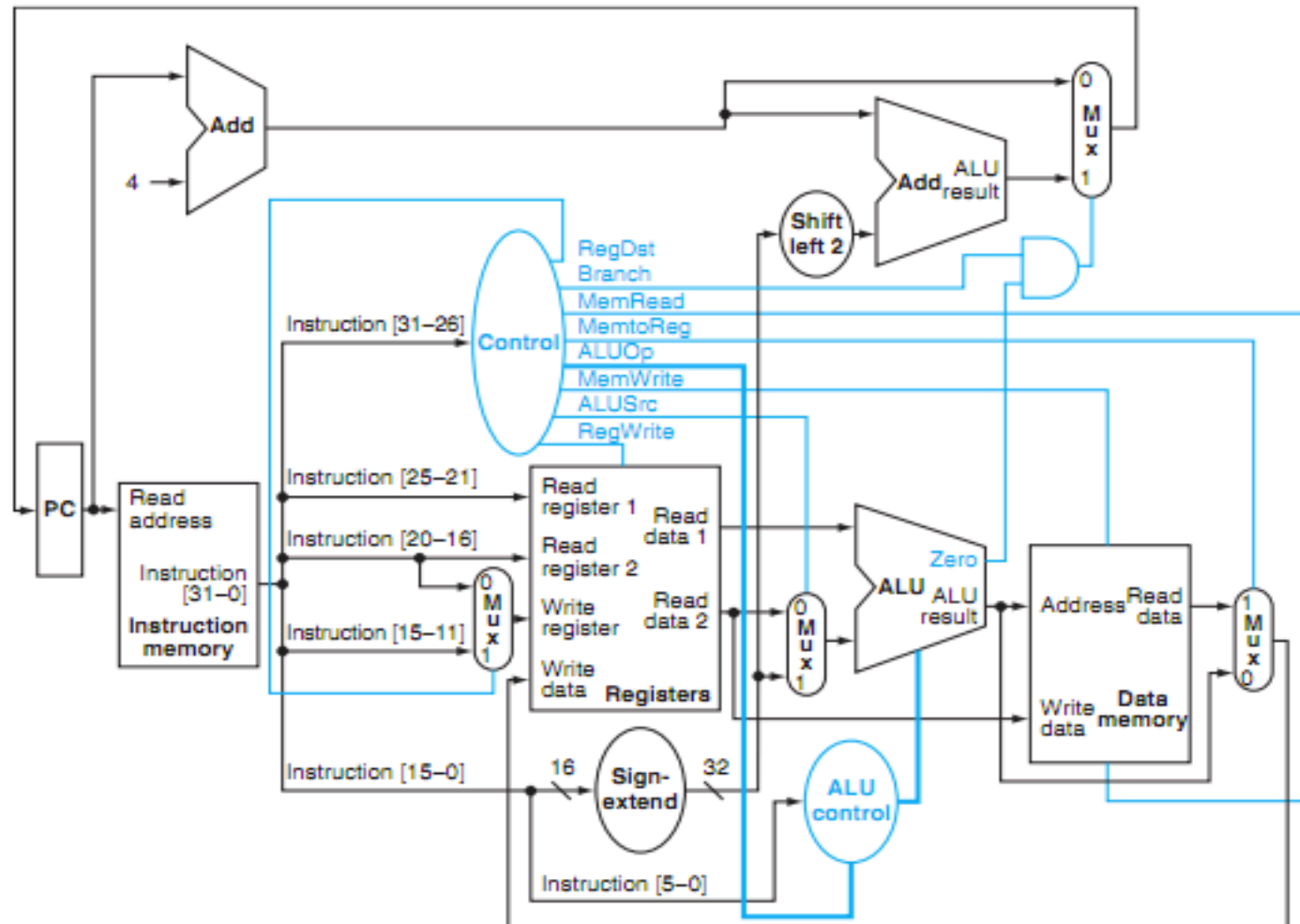

Summary: Single-cycle Processor

- Five steps to design a processor:

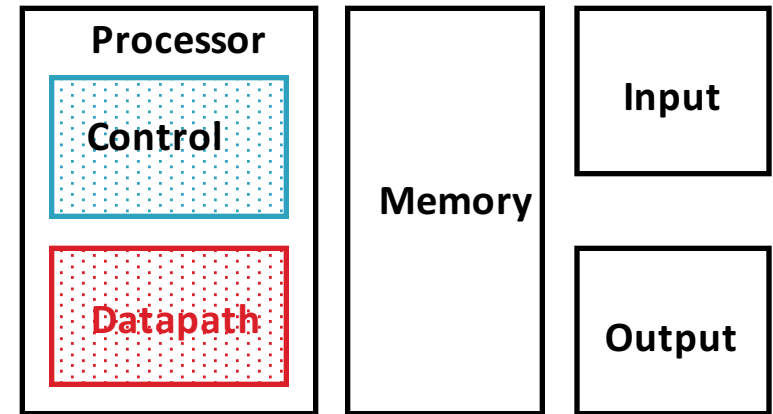1. Analyze instruction set → datapath requirements
2. Select set of datapath components & establish clock methodology
3. Assemble datapath meeting the requirements
4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
5. Assemble the control logic
 - Formulate Logic Equations
 - Design Circuits



Levels of Representation/Interpretation

High Level Language
Program (e.g., C)

Compiler

Assembly Language
Program (e.g., MIPS)

Assembler

Machine Language
Program (MIPS)

*Machine
Interpretation*

Hardware Architecture Description
(e.g., block diagrams)

*Architecture
Implementation*


Logic Circuit Description
(Circuit Schematic Diagrams)

```
temp = v[k];  
v[k] = v[k+1];  
v[k+1] = temp;
```


```
lw  $t0, 0($2)  
lw  $t1, 4($2)  
sw  $t1, 0($2)  
sw  $t0, 4($2)
```

Anything can be represented
as a *number*,
i.e., data or instructions
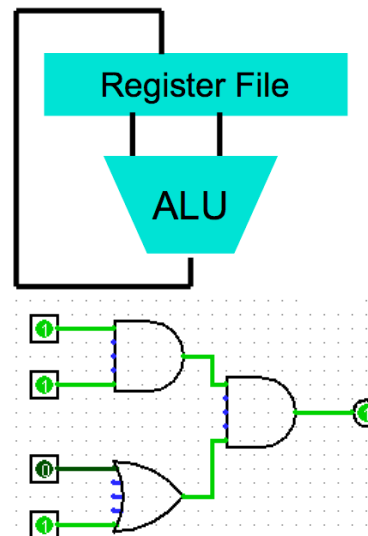
```
0000 1001 1100 0110 1010 1111 0101 1000  
1010 1111 0101 1000 0000 1001 1100 0110  
1100 0110 1010 1111 0101 1000 0000 1001  
0101 1000 0000 1001 1100 0110 1010 1111
```



No More Magic!

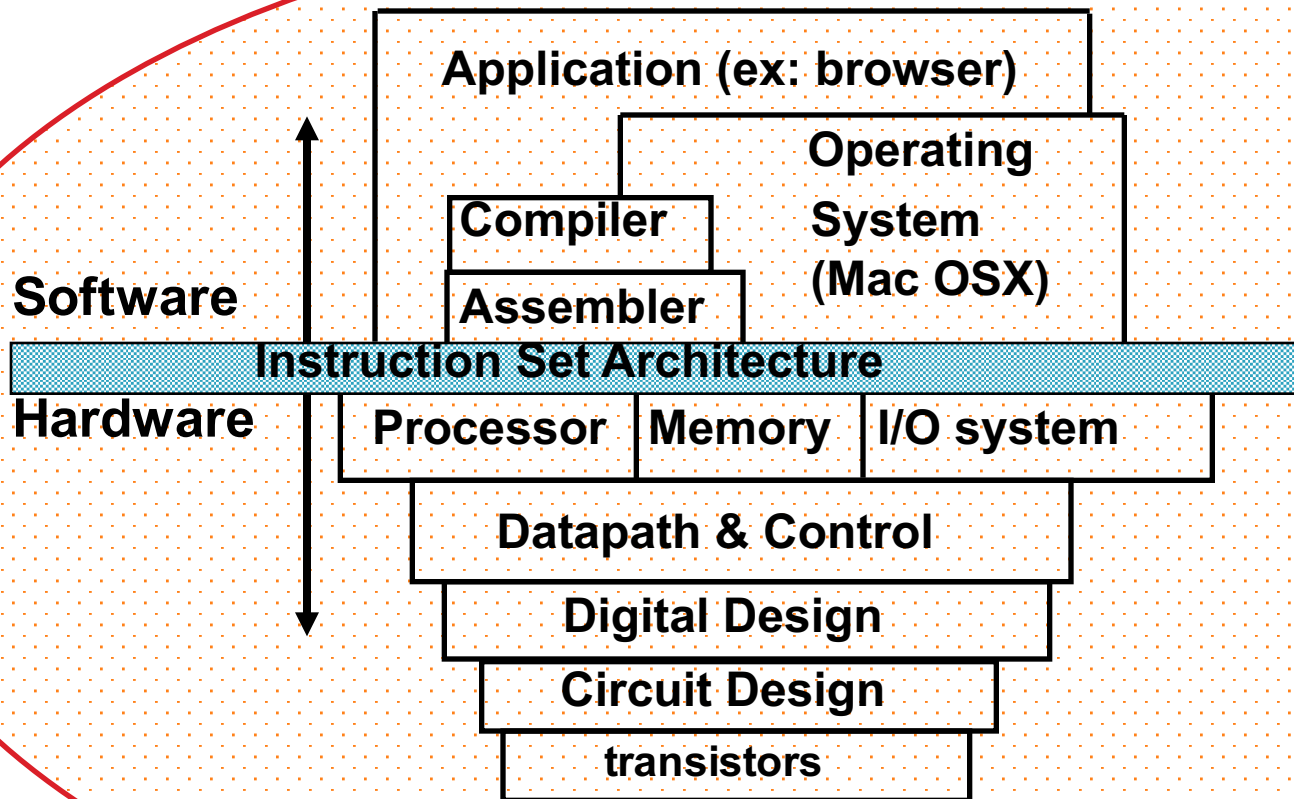

CS61A

CS61B

CS61C ✓

CS61C ✓

CS61C ✓

CS61C ←

CS61C ✓

EE40

Phys 7B